

Voltage across $100\ \Omega$ resistance (V_A)

$$V_A = 2.40V$$

$$i_A = 0.024\ A$$

Expt. No. 2.

Date 03.09.19

Page No. 7

EXPERIMENT-2 - H11/e

AIM: To use mesh and nodal analysis to solve electrical circuits and verify the same.

APPARATUS USED: Resistors ($100\ \Omega$, $56\ \Omega$, $220\ \Omega$, $150\ \Omega$), bread board, connecting wires, multimeter, power supply and digital storage oscilloscope.

a) MESH ANALYSIS:

PROCEDURE:

- Solve the network shown in fig 1 using mesh analysis and compute i_A , i_B and i_C theoretically.
- Obtain the components and connect the network as in figure.
- Measure the currents i_A , i_B , i_C using DSO and verify.
- Observe the KVL and KCL at loops and nodes and verify.
- Repeat the experiment with any other circuit with available components.



CALCULATIONS:

Using KVL in loop 1, 2 and 3

$$\begin{aligned} 5 - 100i_A - 220(i_A - i_B) &= 0 \\ \Rightarrow 5 - 320i_A + 220i_B &= 0 \end{aligned} \quad \text{(loop 1)}$$

$$\begin{aligned} -220(i_B - i_A) - 100i_B - 220(i_B - i_C) &= 0 \\ \Rightarrow 220i_A - 540i_B + 220i_C &= 0 \end{aligned} \quad \text{(loop 2)}$$

Teacher's Signature _____

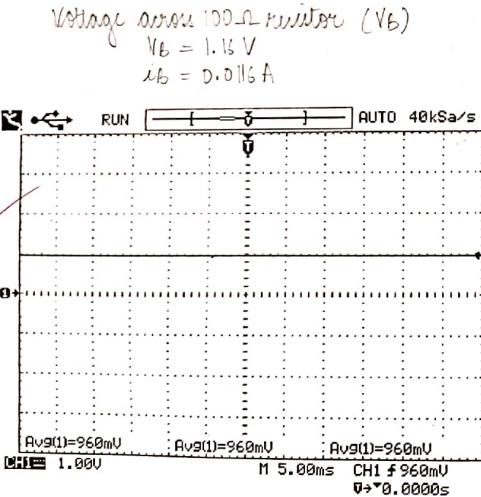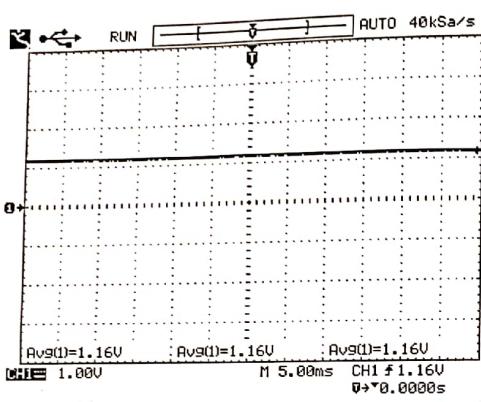

Voltage across 100Ω resistor (V_B)
 $V_B = 1.16 V$
 $i_B = 0.0116 A$

Expt. No. _____

Date _____

Page No. _____

$$-220(i_c - i_B) - 56i_c - 150i_c = 0 \quad \{ \text{loop 3} \}$$

$$\Rightarrow 220i_B - 426i_c = 0 \quad \dots \text{(iii)}$$

In solving (ii), (ii) and (iii),
 $i_A = 0.024 A$, $i_B = 0.0116 A$, $i_C = 0.0064 A$

By practical calculations,

$$V_A = 2.4 V, V_B = 1.16 V, V_C = 960 mV$$

$$i_A = 0.024 A, i_B = 0.0116 A, i_C = 0.0064 A$$

ERROR :

Relative error

$$\Delta i_A = (0.024 - 0.024) A = 0 A$$

0%

$$\Delta i_B = (0.0116 - 0.0116) A = 0.0008 A$$

6.89%

$$\Delta i_C = (0.0064 - 0.0064) A = 0 A$$



0%

b) NODAL ANALYSIS:

PROCEDURE:

1. Solve the network shown in the figure using nodal analysis and compute node voltages at A and B theoretically.
2. Obtain the components and connect the network.
3. Measure the node voltages at A and B using O.S.D and verify.
4. also, observe the KVL and KCL at all loops and nodes and verify.
5. Repeat the experiment with any other circuit with the available components.

Teacher's Signature _____

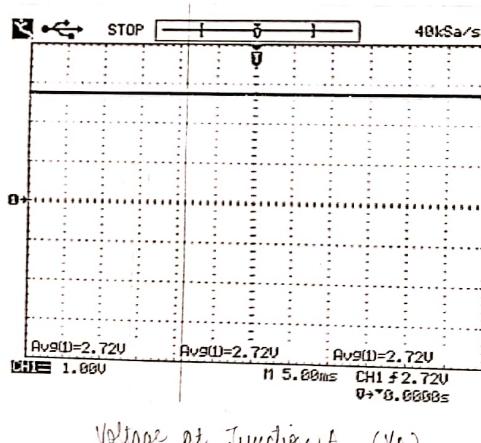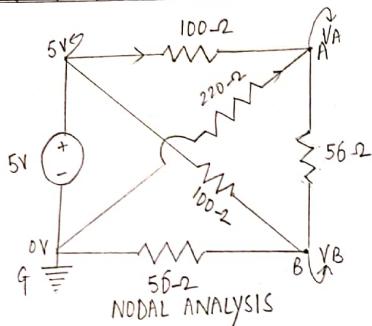

Date _____
Expt. No. _____

Page No. _____

CALCULATION:

Applying KCL at junction A and B,

$$\frac{V_A - 5}{100} + \frac{V_A}{220} + \frac{V_A - V_B}{56} = 0 \quad \{ \text{at A} \}$$

$$\frac{V_B - 5}{100} + \frac{V_B}{56} + \frac{-(V_A - V_B)}{56} = 0$$

on solving, we get

$$V_A = 2.73 \text{ V} \quad V_B = 2.16 \text{ V}$$

By practical experiment,
 $V_A = 2.72 \text{ V}$

$$V_B = 2.20 \text{ V}$$

ERROR:

Relative Error

$$\Delta V_A = |2.72 - 2.73| = 0.01 \text{ V}$$

0.36%

$$\Delta V_B = |2.20 - 2.16| = 0.04 \text{ V}$$

1.85%

RESULTS:


In mesh analysis, the experimental values of $i_A = 0.024 \text{ A}$, $i_B = 0.0116 \text{ A}$, $i_C = 0.0064 \text{ A}$.

In nodal analysis the voltages at two junctions A and B are $V_A = 2.72 \text{ V}$ and $V_B = 2.20 \text{ V}$.


DISCUSSION:

Circuits were solved in this experiment using mesh and nodal analysis. Same circuits were created on a bread



Teacher's Signature _____


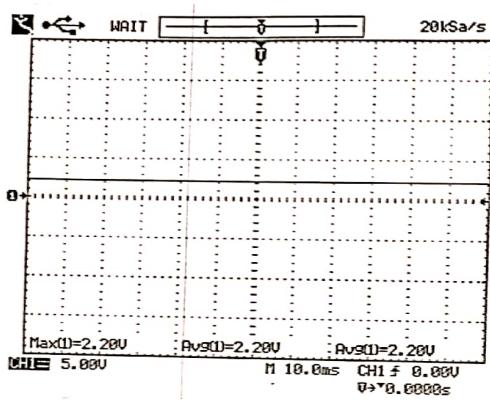


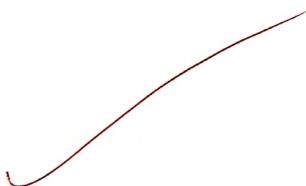... in Voltage at Junction b (V_B)
 $V_B = 2.20V$



	Expt. No. _____	Date _____																		
	Page No. _____																			
<p>board and the measure of current and voltages were confirmed using a DSO.</p> <p>Precautions:</p> <ol style="list-style-type: none"> 1) The connecting wires must be fixed tightly. 2) DSO coupling must be set to D.C. to obtain results. 3) The value of resistances must be checked with a multimeter. <p>CONCLUSION: Kirchoff's voltage and current laws were used to solve the given circuits. Hence, we got the following values:</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%;"></th> <th style="width: 25%; text-align: center;">Experimental</th> <th style="width: 25%; text-align: center;">Theoretical</th> </tr> </thead> <tbody> <tr> <td>a)</td> <td style="text-align: center;">$i_A = 0.024 A$</td> <td style="text-align: center;">$i_A = 0.024 A$</td> </tr> <tr> <td></td> <td style="text-align: center;">$i_B = 0.0116 A$</td> <td style="text-align: center;">$i_B = 0.0116 A$</td> </tr> <tr> <td></td> <td style="text-align: center;">$i_C = 0.0064 A$</td> <td style="text-align: center;">$i_C = 0.0064 A$</td> </tr> <tr> <td>b)</td> <td style="text-align: center;">$V_A = 2.72 V$</td> <td style="text-align: center;">$V_A = 2.73 V$</td> </tr> <tr> <td></td> <td style="text-align: center;">$V_B = 2.20 V$</td> <td style="text-align: center;">$V_B = 2.16 V$</td> </tr> </tbody> </table> <p style="color: red; font-size: 1.5em; margin-left: 10%;">Excellent</p>				Experimental	Theoretical	a)	$i_A = 0.024 A$	$i_A = 0.024 A$		$i_B = 0.0116 A$	$i_B = 0.0116 A$		$i_C = 0.0064 A$	$i_C = 0.0064 A$	b)	$V_A = 2.72 V$	$V_A = 2.73 V$		$V_B = 2.20 V$	$V_B = 2.16 V$
	Experimental	Theoretical																		
a)	$i_A = 0.024 A$	$i_A = 0.024 A$																		
	$i_B = 0.0116 A$	$i_B = 0.0116 A$																		
	$i_C = 0.0064 A$	$i_C = 0.0064 A$																		
b)	$V_A = 2.72 V$	$V_A = 2.73 V$																		
	$V_B = 2.20 V$	$V_B = 2.16 V$																		
Teacher's Signature _____	<u>Debjit</u> 17/1/19																			

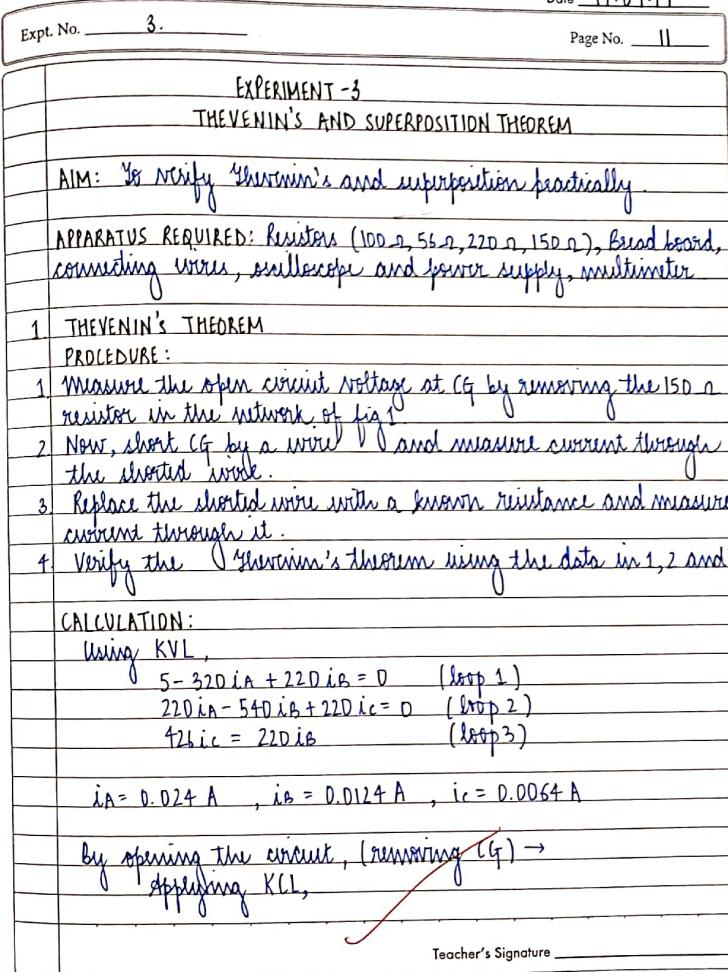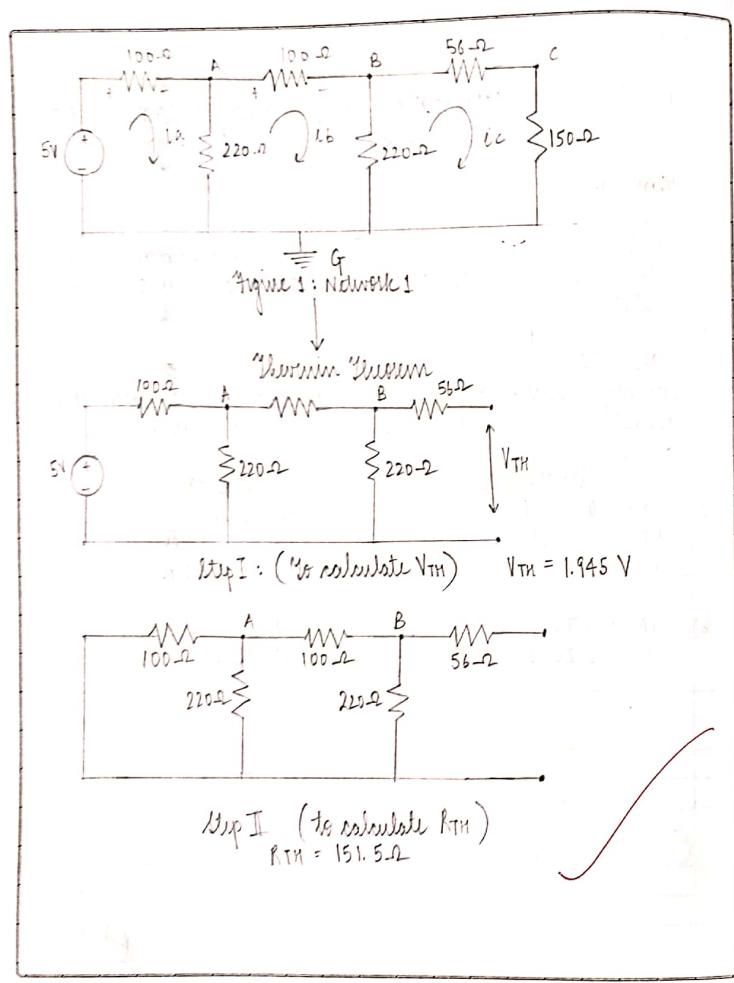

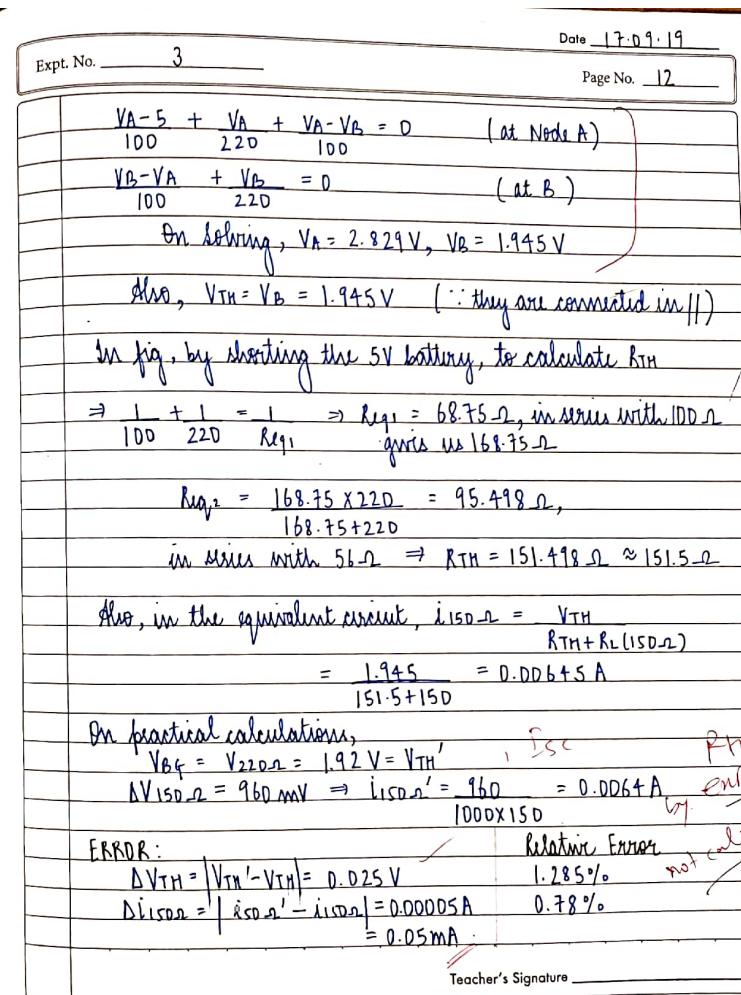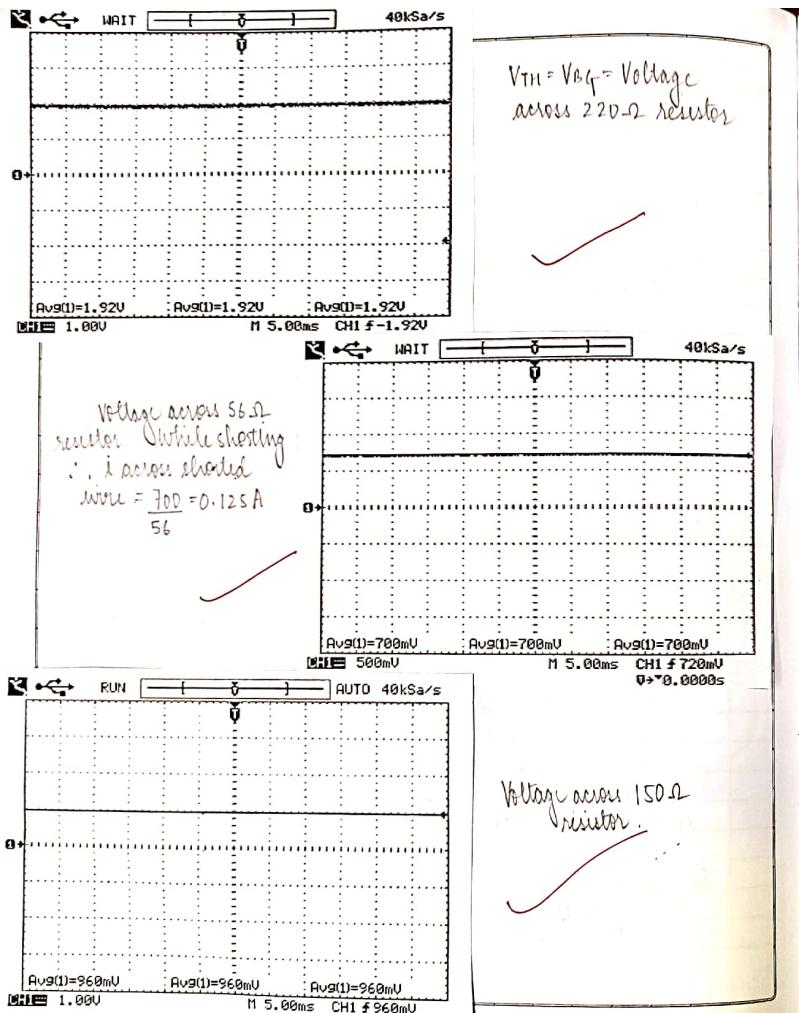

Expt. No. 3

2. SUPERPOSITION THEOREM:

PROCEDURE:

- 1 Connect the circuit as shown in figure and measure i_1 and i_2 respectively.
- 2 also compute the current 'i' in the circuit.
- 3 Verify the superposition theorem from the readings / observations.

CALCULATIONS:

On performing the experiment,

in fig (i), $V_{100\Omega} = 316 \text{ mV}$
 $\Rightarrow i_{100\Omega} = \frac{V_{100\Omega}}{100\Omega} = \frac{316}{100} = 3.16 \text{ mA} = i_1$

In fig (ii), $V'_{100\Omega} = 1.24 \text{ V}$

$\Rightarrow i'_{100\Omega} = \frac{1.24}{100} = 0.0124 \text{ A}$

In fig (iii), $V''_{100\Omega} = -920 \text{ mV}$

$\Rightarrow i''_{100\Omega} = -\frac{920}{100} = -0.0092 \text{ A}$

$i' = i_1 + i_2 = 0.0124 \text{ A} - 0.0092 \text{ A} = 0.0032 \text{ A} = 3.2 \text{ mA}$

FBRDR:

$Ni = |i - i'| = 0.04 \text{ mA}$

$\text{Relative error} = \frac{0.04}{3.16} \times 100 = 1.265 \%$

Teacher's Signature _____


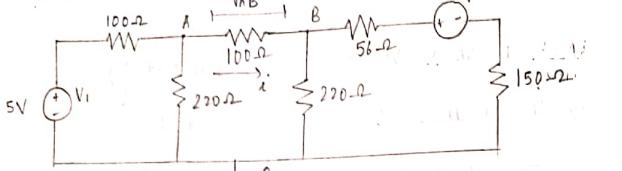
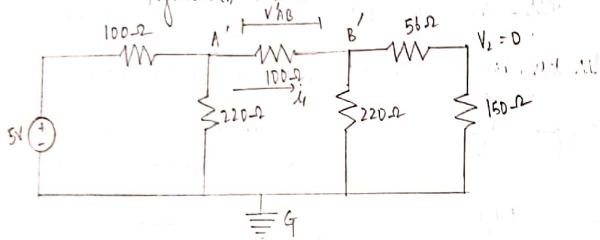
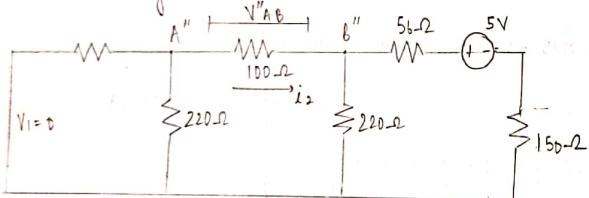
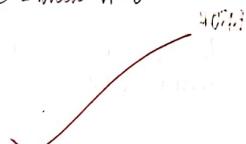


Figure 2(i): Network 2

Figure 2(ii): Network 2 with $V_2 = 0$ Figure 2(iii): Network 2 with $V_1 = 0$ 

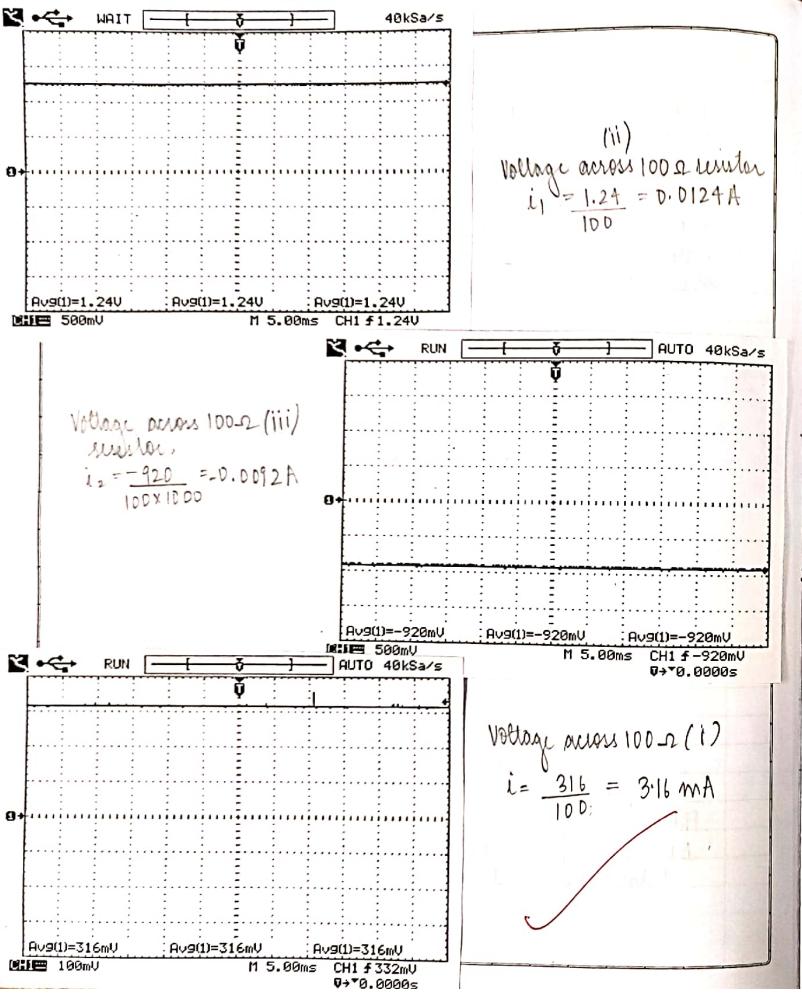

$$(ii)$$

Voltage across 100Ω resistor
 $i_1 = \frac{1.24}{100} = 0.0124 \text{ A}$

Expt. No. 3

Date 17.09.19

Page No. 14

RESULT :

- In the case of Thvenin Theorem,
 $V_{TH}(\text{theoretical}) = 1.945 \text{ V}$, $V_{TH}(\text{practical}) = 1.92 \text{ V}$
 $i_{100\Omega}(\text{theoretical}) = 0.00645 \text{ A}$, $i_{100\Omega}(\text{practical}) = 0.0064 \text{ A}$
- In the case of superposition Theorem,
 $i(\text{using superposition}) = 3.20 \text{ mA}$
 $i(\text{directly}) = 3.16 \text{ mA}$

DISCUSSION:

The Thvenin and the superposition Theorem were used to solve circuits and verified experimentally by measuring voltage and hence current along circuit elements.

Precautions:


- Avoid loose connections in the network.
- Direct contact between wires should be prevented to avoid short circuiting.
- Resistances must be measured carefully.

CONCLUSION:

The Thvenin theorem and superposition theorem are verified using the DSO, within the limits of experimental error, namely 0.78% and 1.265% respectively.

Teacher's Signature _____

[Signature]
20/9/19

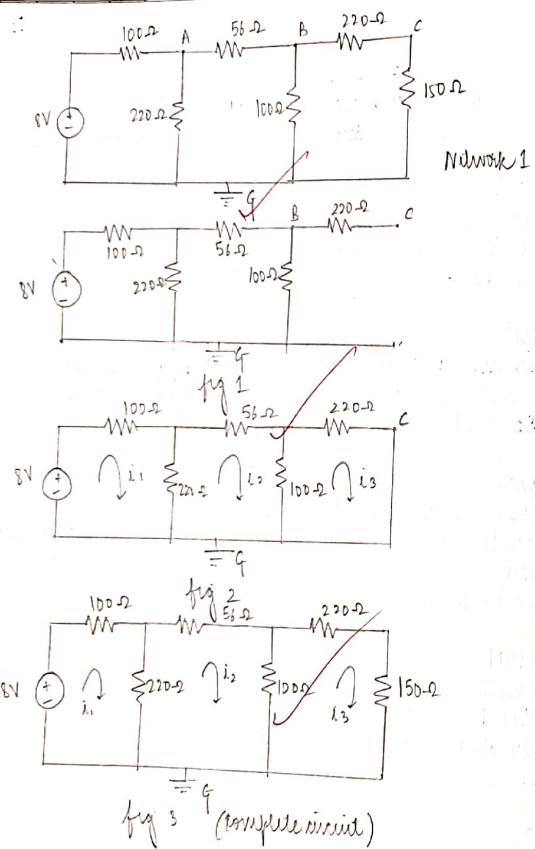

Expt. No. 4

Date 20.09.19

Page No. 15

EXPERIMENT - 4

NORTON'S AND MAXIMUM POWER TRANSFER THEOREM

OBJECTIVE: To verify Norton's and maximum power transfer theorem practically.

APPARATUS USED: Bread board, resistors, connecting wire, power supply, multimeter, oscilloscope.

1. NORTON'S THEOREM:

PROCEDURE:

- 1) Short CG by a wire and measure current through the shorted wire.
- 2) Measure open circuit voltage at CG by removing the 150Ω resistor in fig 1.
- 3) Replace the shorted wire with a known resistance and measure the current through it.
- 4) Verify the Norton's Theorem using data 1, 2, 3.
- 5) Test the same for any other circuit and verify.

CALCULATIONS:


In the circuit, Applying nodal voltage analysis (KCL) at A and B. (fig 1)

$$\frac{V_B}{100} + \frac{V_B - V_A}{56} = 0 \quad (1)$$


$$\frac{V_A - 8}{100} + \frac{V_A}{220} + \frac{V_A - V_B}{56} = 0 \quad (2)$$

$$\text{On solving } V_B = 2.447 \text{ V} = V_{TH} = V_A$$


Teacher's Signature _____

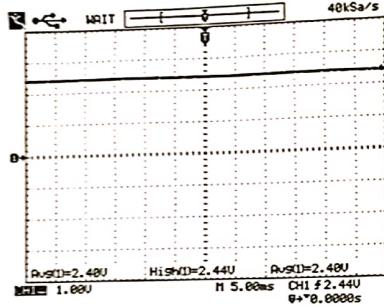
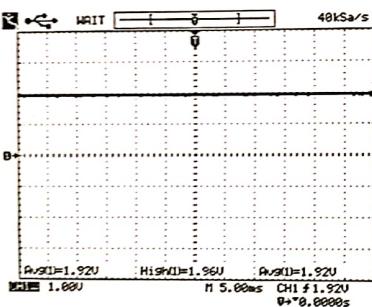
$$V_B = V_{AVG} \approx 100 \Omega \\ = V_{CG} = 2.40V$$


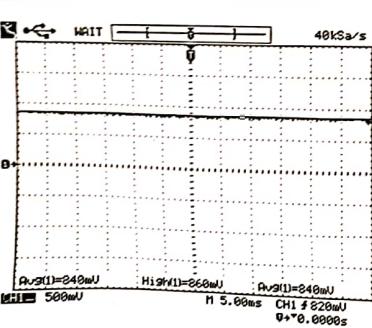
$$V_{AVG} \approx 220 \Omega \\ = 1.92V$$



$$V_{AVG} \approx 150 \Omega \\ = 840 mV$$

Expt. No. _____

Date _____

Page No. _____

Also, calculating $R_{TH} = i_{in}$ from the circuit,

$$R_{TH} = 275.5 \Omega$$

On shorting the CG and solving the circuit, (fig 2)

$$8 - 100(i_1) - 220(i_1 - i_2) = 0 \quad (i)$$

$$- 220(i_2 - i_1) - 56i_2 - 100(i_2 - i_3) = 0 \quad (ii)$$

$$- 100(i_3 - i_2) - 220i_3 = 0 \quad (iii)$$

$$\text{We get, } i_1 = 0.04954 A$$

$$i_2 = 0.02842 A$$

$$i_3 = 8.8824 \times 10^{-3} A = i_{in}$$

$$\text{Voltage across } 220 \Omega, \quad V = (8.8824 \times 10^{-3}) (220) \\ = 1.94128 V$$

$$\text{Also, } R_N = \frac{V_{TH}}{I_{SC}} = \frac{2.40}{8.8824 \times 10^{-3}} = 275.5 \Omega$$

Now,

Replacing shorted wire by a known resistor and measuring current through it, I by applying KVL in (fig 3)

$$8 - 100i_1 - 220(i_1 - i_2) = 0 \quad (i)$$

$$- 220(i_2 - i_1) - 56i_2 - 100(i_2 - i_3) = 0 \quad (ii)$$

$$- 100(i_3 - i_2) - 220i_3 - 150i_3 = 0 \quad (iii)$$

On solving,

$$i_1 = 0.0498 A, i_2 = 0.027 A, i_3 = 5.751 \times 10^{-3} A$$


$$\text{Voltage across } 150 \Omega = 5.751 \times 10^{-3} \times 150 = 862.6 mV$$

$$\text{and } I_1 = \frac{V_{TH}}{R_N + R_L} = \frac{8.824 \times 10^{-3}}{275.5 + 150} \\ = 5.719 \times 10^{-3} A$$

Practically,

$$V_B = V_{CG} = 2.40V, i_{in} = \frac{V_{220}}{220} = \frac{1.92}{220} = 0.0087 A$$

Teacher's Signature _____

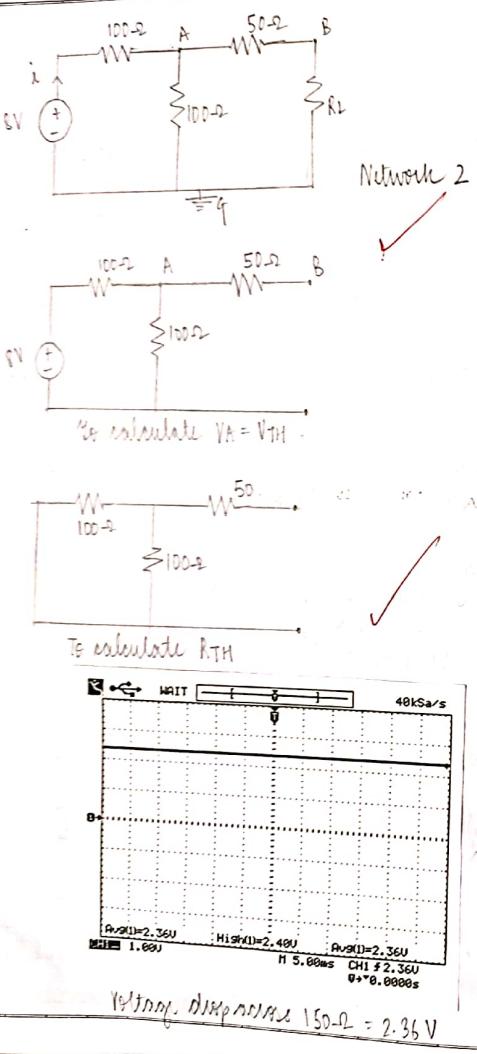

Expt. No. _____

Date _____

Page No. _____

$$i_{150} = \frac{V_{150}}{150} = \frac{840 \text{ mV}}{150} = 5.6 \text{ mA}$$

$$R_N = \frac{V_{TH}}{I_N} = \frac{2.4}{0.00872} = 275.23 \Omega \quad I_1 = \frac{R_N}{(R_N + R_L)} \times I_N \\ = \frac{0.087 \times 275.23}{275.23 + 150} = 5.631 \text{ mA}$$

ERROR:

Relative Error

$$\Delta V_R = |V_T - V_P| = |2.447 - 2.40| = 0.047 \text{ V}$$

1.92%

$$\Delta I_N = |\Delta I_T - \Delta I_P| = |8.882 - 8.72| = 0.162 \text{ mA}$$

1.82%

$$\Delta I_{150} = |I_{T_{150}} - I_{P_{150}}| = |5.751 - 5.6| = 0.151 \text{ mA}$$

2.62%

2. MAXIMUM POWER TRANSFER THEOREM:

PROCEDURE:

- In the circuit, derive the value of load resistance R_L required for maximum power transfer.
- Obtain the component and connect the circuit for various values of R_L including the value obtained in Step I.
- Compute the input power, output power, and efficiency for different R_L and verify the maximum power transfer theorem.


CALCULATIONS:

In the circuit, opening R_L and applying KCL at A,


$$\frac{V_A}{100} + \frac{V_A - 8}{100} = 0$$

$$\Rightarrow \frac{V_A}{50} = \frac{8}{100} \quad \Rightarrow \quad V_A = 4V$$


Teacher's Signature _____

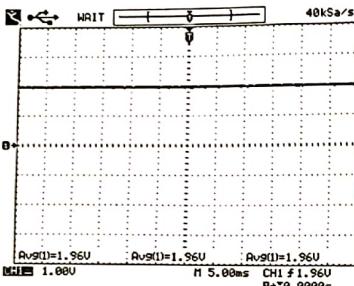

Voltage drop
across 100Ω
= 1.96 V

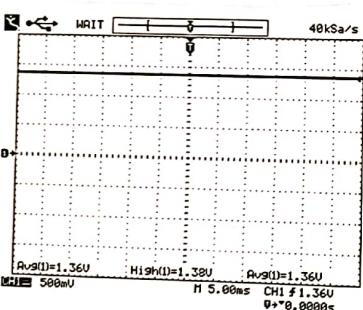

Voltage drop
across 56Ω
= 1.36 V

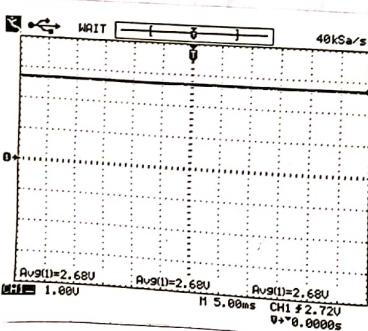

Voltage drop
across 220Ω
= 2.68 V

Expt. No. _____

Date _____

Page No. _____

$\therefore V_{TH} = V_A = 4V$ and shorting 8V source to calculate R_{TH} , we get

$$R_{TH} = \frac{(100 + 56)}{2} = 100\Omega$$

\therefore by Maximum Power Transfer Theorem, $R_L = R_T = 100\Omega$
(as $P_{VAL} = \frac{R_L}{R_L + R_{TH}} \cdot V_{TH}^2$)

$$\Rightarrow P_{AL} = \frac{(V_{RL})^2}{R_L} = \frac{V_{TH}^2 \cdot R_L}{(R_L + R_{TH})^2 \cdot R_L} = \frac{16 \cdot R_L}{(R_L + 100)^2}$$

$$\text{for maxima, } \frac{dP_{AL}}{dR_L} = 0 \Rightarrow R_L = 100\Omega$$

OBSERVATIONS:

For a source voltage $V = 8V$.

S.No.	$R_L(\Omega)$	$i(A)$	$P_{input}(W)$	$V_{RL}(V)$	$P_{output}(W)$	Efficiency ($\frac{P_{out}}{P_{out}}$ × 100)
1.	150	0.048	0.384	2.36	0.0371	9.66%
2.	100	0.050	0.4	1.96	0.0384	9.60%
3.	56	0.059	0.472	1.36	0.033	6.99%
4.	220	0.046	0.368	2.68	0.032	8.87%

RESULT:

- Hence, we can see that the maximum power across the output is obtained at $R_L = 100\Omega$. Hence, maximum power theorem is verified.
- In the case of Norton's theorem,

Teacher's Signature _____

Expt. No. _____

Date _____

Page No. 19

$$V = V_{CC} = 2.40 \text{ V}$$

$$i_N = \frac{V_{220}}{220} = 0.00872 \text{ A}$$

$$I_L = \left(\frac{R_N}{R_N + R_L} \right) I_N = 5.631 \text{ mA} \quad (\text{Using Norton equivalent})$$

$$\text{and practically, } I_L = I_{150} = \frac{V_{150}}{150} = 5.6 \text{ mA}$$

Error in $I_L = \Delta I_L = 0.031 \text{ mA}$, % error = 0.55%

Hence, Norton's Theorem is verified.

DISCUSSION:

Precautions and sources of error:

1. Avoid loose connections in network.
2. Direct contact between wires should be prevented to avoid short circuiting.
3. Resistances should be measured carefully. In the case of max power theorem, 56- Ω resistor was used in place of 50- Ω which may have caused slight deviation in the calculations.

CONCLUSION:

Norton's Theorem and Maximum Power Transfer Theorem were verified practically within experimental limits with error as indicated.

Calculations are to
be done in Thevenin
equivalent circuit.

1/10/19.

9.5
10

Teacher's Signature _____


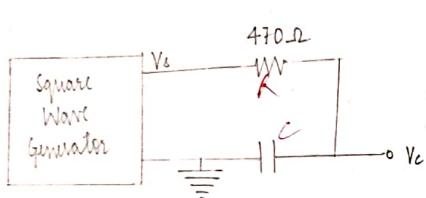


Figure 1A

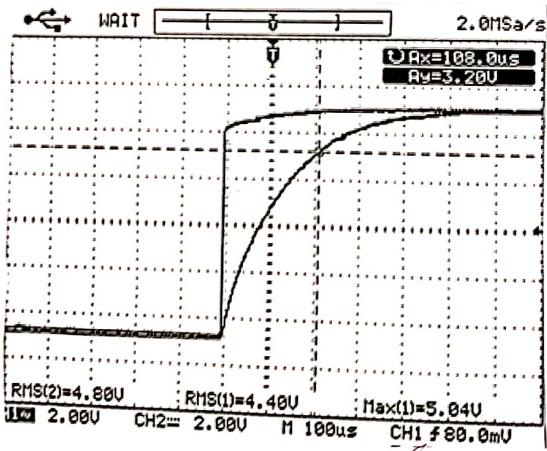

$V_{Cmax} = 5.04V$
 $3.185V \text{ reached in } 108\mu s$

Date 8.10.19
 Expt. No. 5.

Page No. 20

EXPERIMENT-5

RC AND RL TRANSIENT ANALYSIS

- AIM: (1) To observe and take the complete response of an RC and RL circuit to step input.
 (2) To determine the time constant and check with the theoretically calculated value.

APPARATUS: Square wave generator, DSO, resistor, capacitor, inductor, connecting wires, bread board.

1 RC CIRCUIT:

PROCEDURE:

- 1 Connect the circuit as shown in fig 1A. Observe and trace the waveform appearing on the DSO. Set the frequency in range 200 - 500 Hz.
- 2 Verify theoretically.

CALCULATIONS:

$$T_{theoretical} = RC = 470 \times 0.22 \times 10^{-6}$$

$$= 103.4 \times 10^{-6} \text{ s}$$

Pick voltage, $V_{Cmax} = 5.04V$
 Voltage reached in 1 time constant, i.e.,
 $T_{seconds} = 63.2\% \text{ of } 5.04V$
 $= 3.185V$

$$T_{experimental} = 108\mu s$$

$$= 108 \times 10^{-6} \text{ s}$$

Teacher's Signature _____


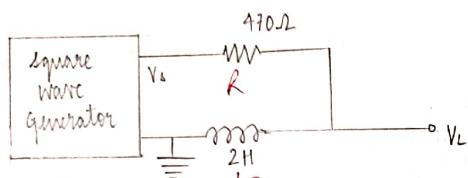


Figure 2A

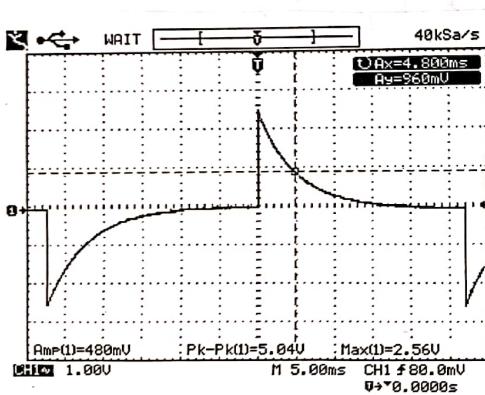

$V_{L\text{max}} = 2.56 \text{ V}$
947.2 mV reached in 4.8 ms

Date _____
Expt. No. _____

Page No. _____

ERROR:

$$\text{Error in } T_{RL} = |103.4 \times 10^{-6} - 108 \times 10^{-6}| \\ = 4.6 \times 10^{-6}$$

Relative error = 4.45% ✓

2) RL CIRCUIT:

PROCEDURE:

- 1) Connect the circuit as shown in fig 2A. Observe and trace the waveform appearing on the oscilloscope. Set frequency in range 200-500 Hz.
- 2) Verify T theoretically.

CALCULATIONS:

$$T_{\text{theoretical}} = \frac{L}{R} = \frac{2}{470} = 4.26 \times 10^{-3} \text{ s}$$

Peak voltage = 2.56 V

Voltage reached in 1 time constant, i.e. T seconds,
= 37% of 2.56 V
= 947.2 mV ✓

$T_{\text{experimental}} = 4.8 \text{ ms}$ ✓

ERROR:

$$\text{Error in } T_{RL} = |4.26 \times 10^{-3} - 4.8 \times 10^{-3}| \\ = 0.54 \times 10^{-3}$$

Relative error = 17.67% ✓

Teacher's Signature _____

RESULT: The time constant τ in the RC circuit is $108 \mu\text{s}$, with an error of 4.45% from the theoretical value ($103.4 \mu\text{s}$). In RL circuit, it is $4.8 \times 10^{-3} \text{ s}$, with an error of 12.67% from the theoretical value ($4.26 \times 10^{-3} \text{ s}$).

DISCUSSION:


Precautions and Sources of Error:

1. The square waveform from the function/pulse generator may be checked on DSO and adjusted to proper size before applying it to the circuit.
2. The connections might become loose during the experiment which results in vague readings.
3. Constant voltage supply across the resistor results in heating which affects readings.
4. Exact values were difficult to reach using the tracker.


CONCLUSION:

Hence, the response of an RC and RL circuit was observed on the DSO. The time constants were determined and compared with theoretically calculated values within experimental limits.


~~Vikram
22/10/19~~ ①

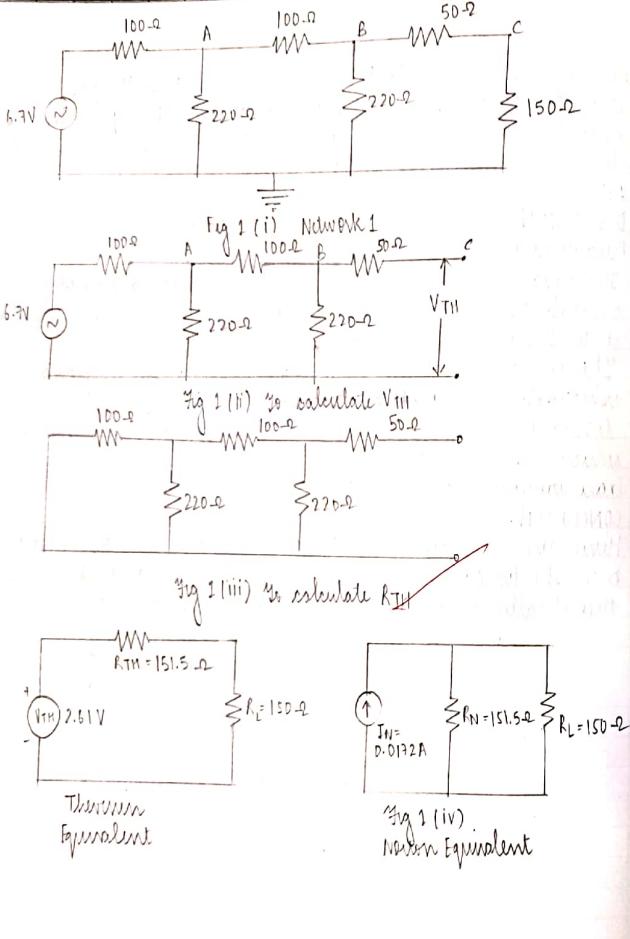

Expt. No. 6.		Date 15.10.19
		Page No. 23
EXPERIMENT-6		
THEVENIN'S, NORTON'S AND SUPERPOSITION THEOREM IN AC CIRCUITS		
AIM: To verify Thevenin's, Norton's and superposition theorem practically.		
APPARATUS: Board board, resistors, connecting wire, AC power supply, transformer, DC power supply, multimeter, oscilloscope, pen diode.		
THEVENIN'S AND NORTON'S THEOREM:		
PROCEDURE:		
<ol style="list-style-type: none"> Measure open circuit voltage at CG by removing the 150Ω resistor in the wire in fig 1 Now short CG by a wire and measure current through the shorted wire. Replace the shorted wire with a known resistance and measure the current through it. Verify the Thevenin's and Norton's theorem using the data 1, 2, 3. 		
CALCULATIONS:		
Theoretically, a) Thevenin's Theorem To find V_{TH} from fig 1 (ii), by applying KCL, $\frac{VA - 6}{100} + \frac{VA}{220} + \frac{VA - VB}{100} = 0 \quad \dots (1)$ $\frac{VB - VA}{100} + \frac{VB}{220} = 0 \quad \dots (2)$		
Teacher's Signature _____		

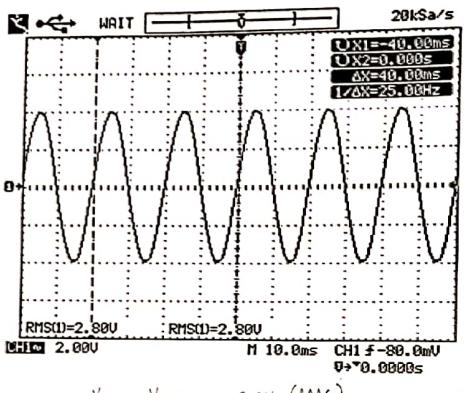
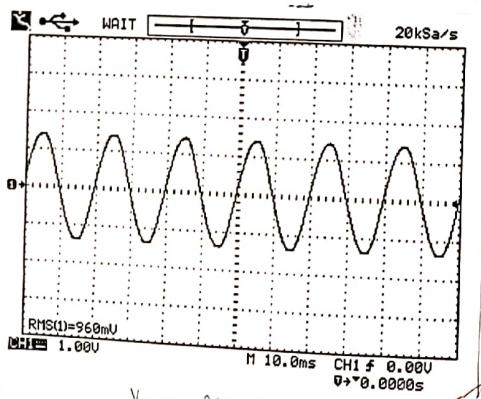
$$V_{CQ} = V_{220\Omega} = 2.8V \text{ (rms)}$$



$$V_{S6\Omega} = 960mV$$

Expt. No. _____

Date _____

Page No. _____

from Q and Q, $V_A = 3.791V$, $V_B = V_{TH} = 2.61V$

thus, calculating R_{TH} from fig 1(iii), $R_{TH} = 151.5\Omega$

$$\therefore i_{\text{parallel}} (\text{across } 150\Omega) = \frac{V_{TH}}{R_{TH} + 150} = \frac{2.61}{151.5 + 150} = 8.65 \text{ mA}$$

Practically,
 $i_{150} = \frac{V_{150}}{150\Omega} = \frac{1.32}{150} = 8.8 \text{ mA}$ (directly)

$$V_{TH} = V_{CQ} = V_{220\Omega} = 2.8V$$

$$i_{SC} = i_{S6\Omega} = \frac{V_{S6\Omega}}{56\Omega} = \frac{960mV}{56} = 17.14 \text{ mA}$$

$$\therefore R_{TH} = V_{TH} = \frac{2.8}{17.14 \times 10^{-3}} = 163.3\Omega$$

$$i_{150} = \frac{V_{TH}}{R_{TH} + 150} = \frac{2.8}{163.3 + 150} = 8.93 \text{ mA}$$

Errors:

$$1) \Delta i_{150} = |i_{TH} - i_p| = |8.65 - 8.8| = 0.15 \text{ mA}$$

$$\% \text{ error} = \frac{0.15}{8.8} \times 100 = 1.73\%$$



2) for practical justification,


$$\Delta i_{150} = |8.93 - 8.8| = 0.13 \text{ mA}$$

$$\% \text{ error} = \frac{0.13}{8.8} \times 100 = 1.45\%$$


b) Norton's theorem

Teacher's Signature _____

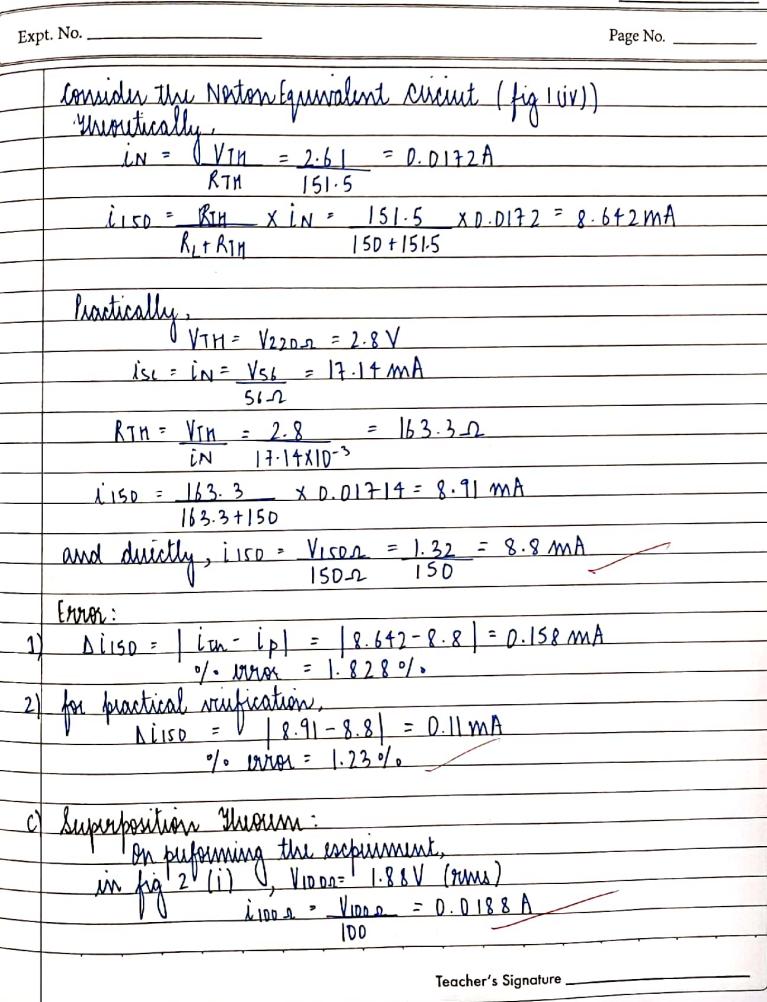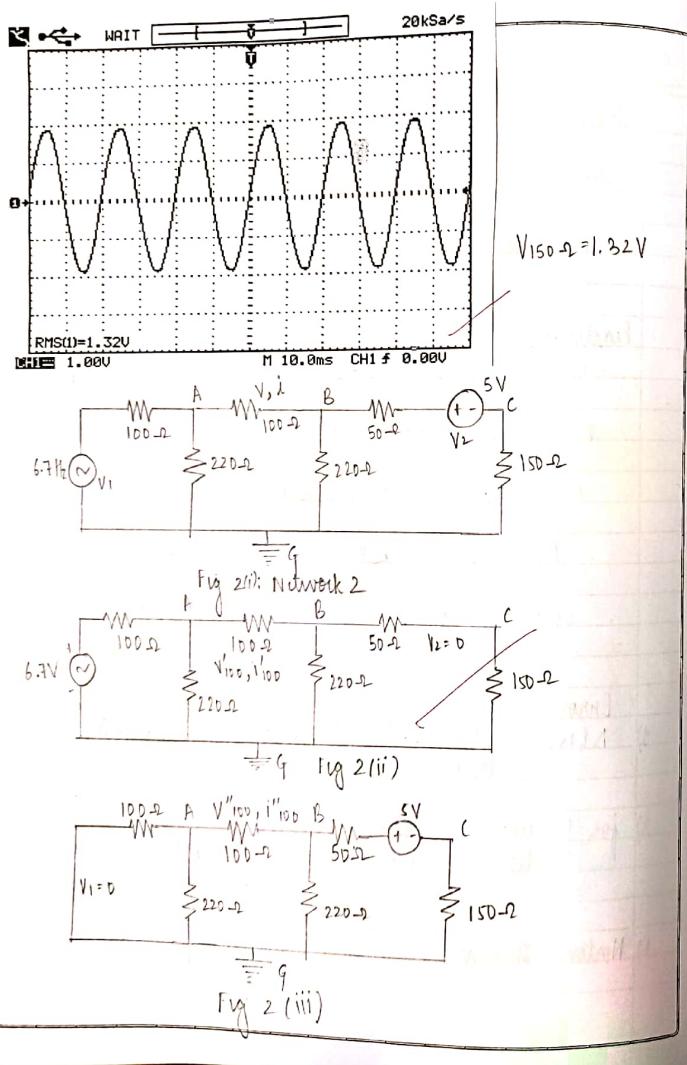

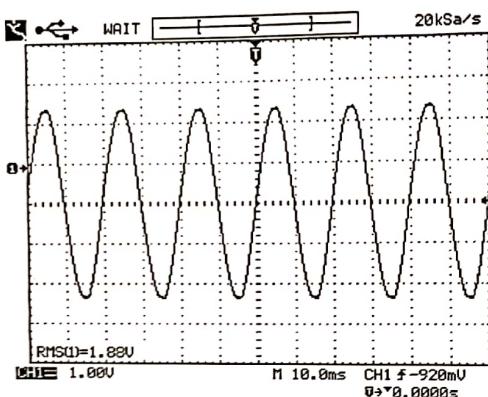

$$V_{100n} = 1.28V \text{ (fig 2(i))}$$

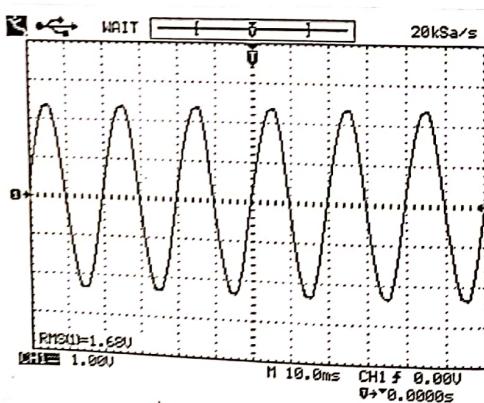

$$V_{100nL} = 1.68V \text{ (fig 2(ii))}$$

Date _____
Expt. No. _____

Page No. _____

in fig 2 (ii), $V'_{100n} = 1.68V$ (rms)

$$i'_{100} = \frac{V'_{100}}{100} = 0.0168A$$

in fig 2 (iii), $V''_{100n} = -920mV$ (avg)

$$i''_{100} = \frac{-920 \times 10^{-3}}{100} = -0.0092A$$

from (ii) and (iii), by superposition principle

$$i_{100n} = \sqrt{(i'_{100})^2 + (i''_{100})^2} = \sqrt{(0.0168)^2 + (0.0092)^2} = 0.0191A$$

Error:

$$\Delta i_{100n} = |0.0191 - 0.0188| = 0.0003A$$

$$\% \text{ error} = 1.57\%$$


PROCEDURE FOLLOWED:

- 1) Connect the circuit as shown in diagram (fig (i),(ii),(iii)) and measure the currents i'_{100} and i''_{100} respectively.
- 2) Also compute the current i in the circuit of diagram.
- 3) Verify superposition theorem from the reading / observations.
- 4) Test the same for any other circuit and verify.

RESULTS:

"Kirchhoff's, Newton's and Superposition Theorem are verified for given AC circuits with errors of 1.45%, 1.23% and 1.57% respectively."

Teacher's Signature _____

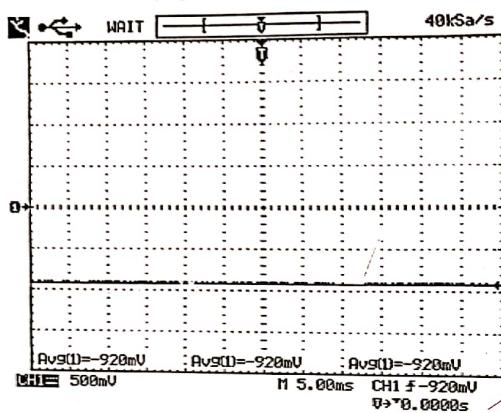

Expt. No. _____

Date _____

Page No. 27

DISCUSSION:

Incantations and sources of error:


1. The value of the resistances must be carefully checked before use.
2. Transformer was used for AC power supply of 6.7 V (rms) for isolation.
3. For AC value, RMS values were taken while for DC values, avg values were taken.

CONCLUSION:

Thus, Kirchhoff, Norton and superposition theorem were successfully verified within experimental errors.

✓
02/10/19
10

Teacher's Signature _____

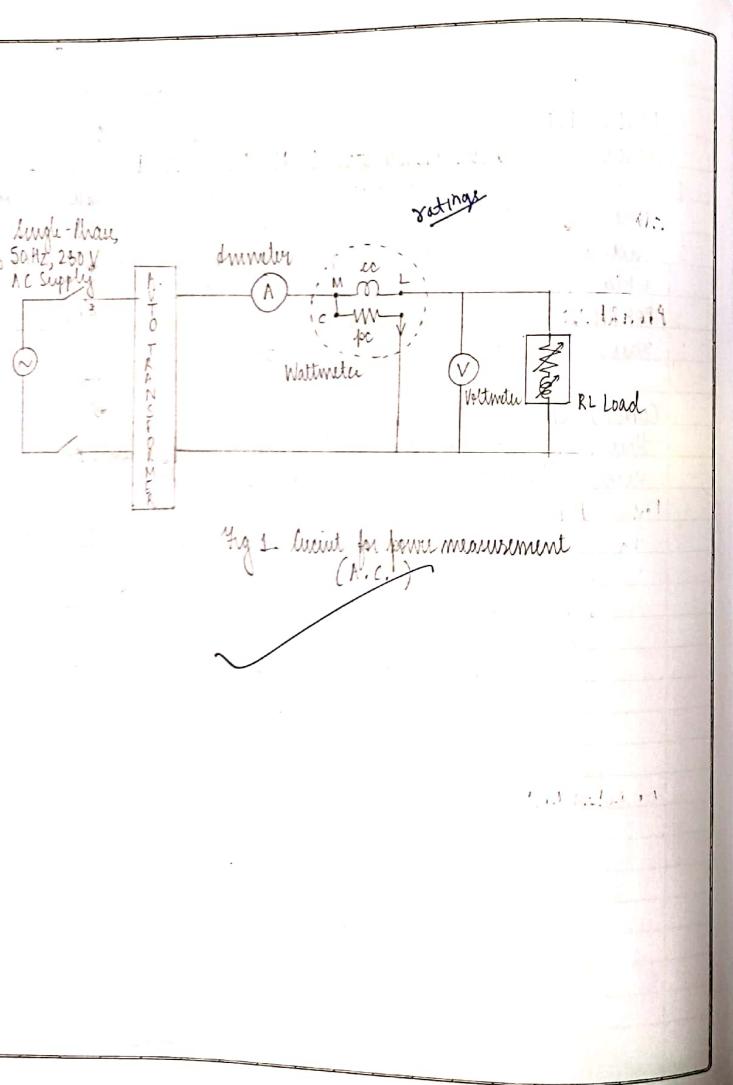

Date 22.10.19
Expt. No. 7.
Page No. 28

EXPERIMENT - 7 POWER MEASUREMENT IN AC CIRCUITS

AIM: Single-phase circuit power measurement using one Wattmeter
Method:

APPARATUS:

- 1) Moving iron Ammeter (0-5A)
- 2) Moving iron Voltmeter (0-500V)
- 3) ElectroDynamics Wattmeter (0-300W)
- 4) Choke Coils and resistance

PROCEDURE:

- 1) Make the connections as shown in the figure for both Resistive and R-L loads. If the current coil of wattmeter can't carry the load current use a current transformer in conjunction with it.
- 2) For a particular set up of RL load note the meter readings. Do the same for resistive loads.
- 3) Calculate the power factor in both the cases.

CALCULATIONS:

- a) $P.F. = \frac{\text{Power (Watt)}}{\text{Apparent power (VA)}}$
where Apparent power = Voltmeter reading \times Ammeter reading
- b) Power = Wattmeter reading \times Multiplying factor of wattmeter

Teacher's Signature _____

OBSERVATIONS:

Multiplying factor of wattmeter = 2

S.No.	Volts (V)	Amps (A)	Watt (W)	Apparent Power (VA)	P.F.	Error	Nature of Load
1.	230	1.00	105	230.00	0.913	8.7%	Resistive
2.	228	2.91	325	663.48	0.98	2%	Resistive
3.	227	3.90	440	885.30	0.994	0.59%	Resistive

Multiplying factor of wattmeter = 4

S.No.	Volts (V)	Amps (A)	Watt (W)	Apparent Power (VA)	P.F.	Nature of Load
1.	230	0.28	12	64.4	0.745	R-L
2.	230	0.66	24	151.8	0.632	R-L
3.	228	0.76	30.5	173.28	0.704	R-L

Calcs?

Date 22.10.19

Page No. 29

Expt. No. 7

RESULT:

- The power factor for the resistive circuit is 0.9623 (mean) with a deviation (mean) of 3.76% from ideal value (1).
- The power factor for the R-L load circuit is 0.693 (mean).

DISCUSSION:

Power measurement of AC circuits is an important process due to the extensive application in everyday life. The power factor calculation indicates that for a Resistive circuit, p.f. is nearly 1 (ideally, equal to 1) while for R-L load, it generally lies between 0.3 - 0.8.

Precautions and Sources of Error:

- The circuit was operating at high voltage of 230V. Thus, safety measures were taken to prevent shock.
- Connections should not be loose.

CONCLUSION:

Hence, power measurements were performed on A.C. circuits and power factors were calculated as indicated.

Teacher's Signature

20/10/19

Expt. No. 8

EXPERIMENT-8

AIM: Three-phase circuit power measurement using two wattmeter method.

APPARATUS:

- 1) Moving Iron Ammeter (0-5A)
- 2) Moving Iron Voltmeter (0-500V)
- 3) Electrodynamics Wattmeters (0-300W)
- 4) choke coil and resistors

PROCEDURE:

- 1) Make the connections as shown in the figure on the left side.
- 2) First measure the power with resistive load and in this case two-wattmeter reading will be the same.
- 3) connect the choke coil of some inductance in each phase.
- 4) increase or decrease the inductances by equal amounts and record the meter readings.
- 5) calculate the power factor by calculations shown below.


CALCULATIONS:

Real Power is the wattmeters' reading sum multiplied by the multiplication factor for that configuration.

Power of one wattmeter be W_1 and second wattmeter be W_2 .

Real Power = $(W_1 + W_2) \times M.F.$
Also, real power for a 3- ϕ A.C. circuit using two-wattmeter method is $\sqrt{3} V_L I_L \cos \phi$, V_L is line voltage, I_L is line current

Teacher's Signature _____

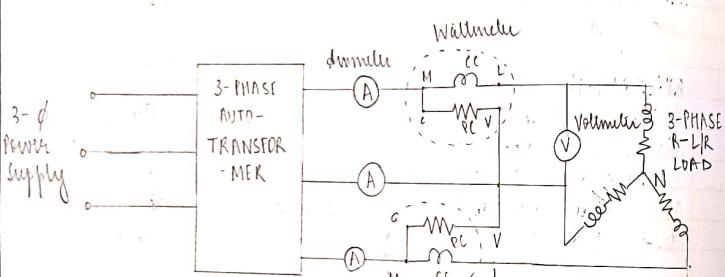

CIRCUIT DIAGRAM FOR POWER MEASUREMENTS

$$\text{Apparent Power} = \sqrt{3} V_L I_L$$

$$\therefore \text{Power Factor} = \frac{\text{Real Power}}{\text{Apparent Power}} = \cos \phi$$

Power factor is to be calculated by $P.F. = \frac{W}{\sqrt{3} V_L I_L}$, $W = W_1 + W_2$

Take obs 1 where $V_L = 440V$, $I_L = 1.05A$

$$W_1 = 110W, W_2 = 90W \Rightarrow W = W_1 + W_2 = 200W, M.F = 4$$

$$P.F = \frac{200 \times 4}{\sqrt{3} \times 440 \times 1.05} = 0.997$$

Similarly, P.F is calculated for other readings.

RESULT:

- 1) The power factor for the resistive circuit on average is 0.99358 with a deviation (mean) of 0.64% from ideal value.
- 2) Power factor for the R-L load circuit (mean) is

ERROR IN MEASUREMENT OF POWER FACTOR

S.No.	Power Factor	Error	Relative Error
1.	0.999	$ 1 - 0.999 = 0.001$	0.1%
2.	0.989	$ 1 - 0.989 = 0.011$	1.1%
3.	0.992	$ 1 - 0.992 = 0.008$	0.8%

Error in the avg p.f. for resistive load circuit

$$= \left(\frac{|1 - 0.99358|}{1} \times 100 \right) \%$$

$$= 0.642\%$$

✓

EXPERIMENT - 9

OBJECTIVES:

- 1) To study the constructional details of a single-phase transformer.
- 2) To display the B-H curve for the core material used on an oscilloscope.
- 3) Waveforms of exciting current and induced voltage at different flux levels.


APPARATUS:

1. Transformer under test
2. Single phase two winding transformers with tappings to be used as an isolated supply for the experiment.
3. Oscilloscope; multimeter
4. A rheostat, with a current rating more than no load current of the transformer under test.
5. Two voltmeters, one with voltage range equivalent to the full voltage rating and the other with 10% of the voltage rating and the other with one multi-range.
6. Two ammeters, one with current range equivalent to full load current rating and the other with multi-range.
7. Load to be used on the secondary.
8. A 0.5 or 1 watt resistance of the order of 1 mega ohm and a mica or paper capacitor of the order of 1 micro F for making an integrating circuit.
9. Single phase auto-transformer with full load current rating.

THEORY:


A single-phase transformer essentially consists of two

Teacher's Signature _____

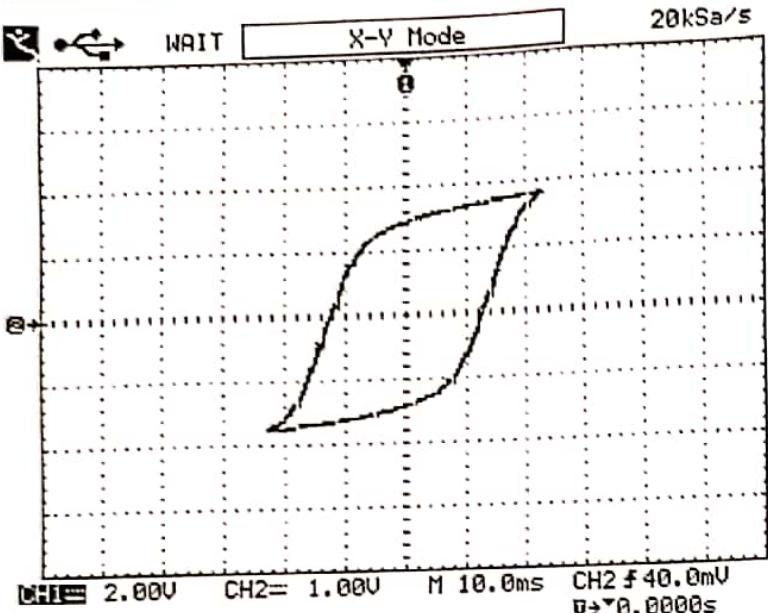


$V = 172.5 \text{ V}$
 $R = 23.6 \Omega$

✓

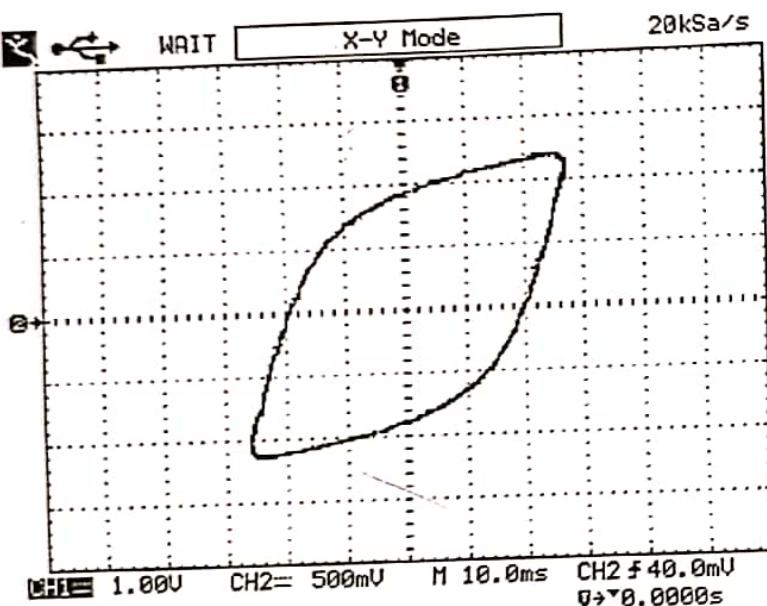


$V = 115 \text{ V}$
 $R = 23.6 \Omega$

✓

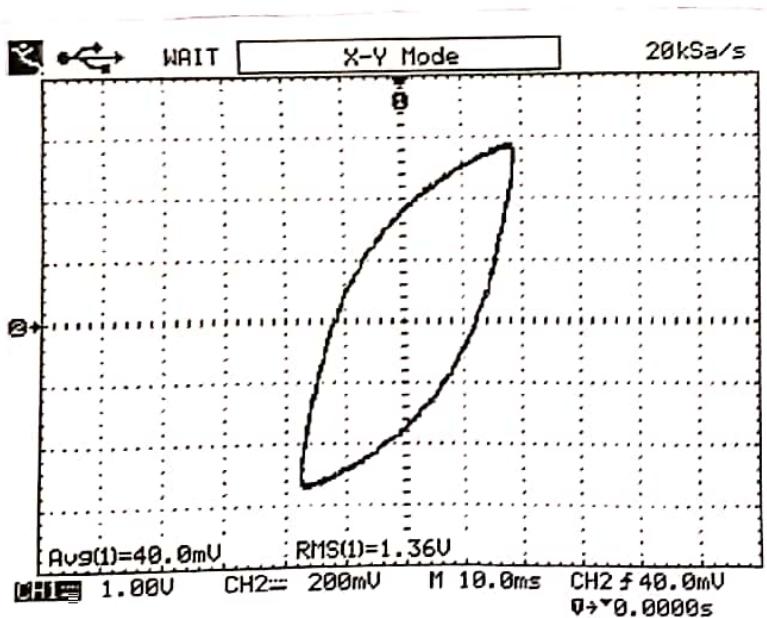

~~$V = 54.5 \text{ V}$~~
 ~~$R = 23.6 \Omega$~~


✓

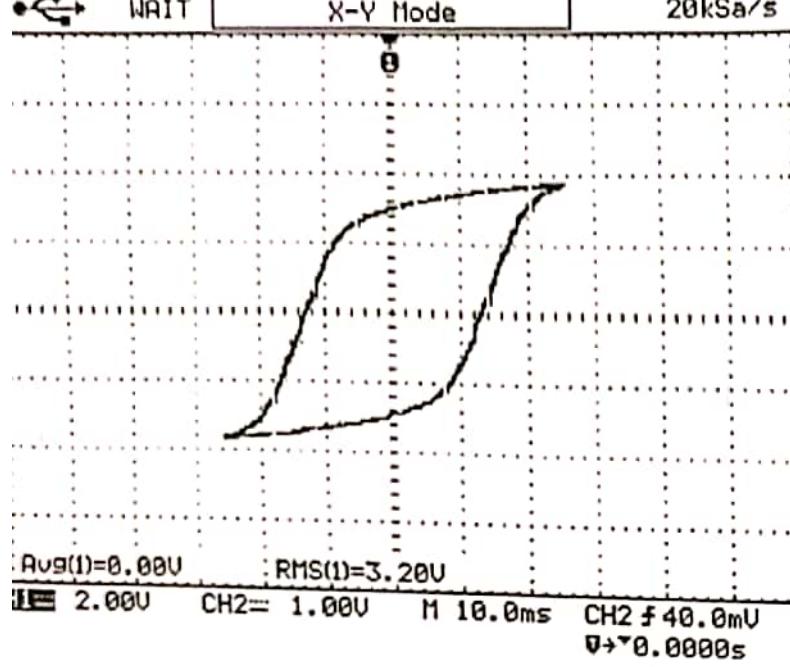

$$V = 180V$$

$$R = 23.6\Omega$$


✓

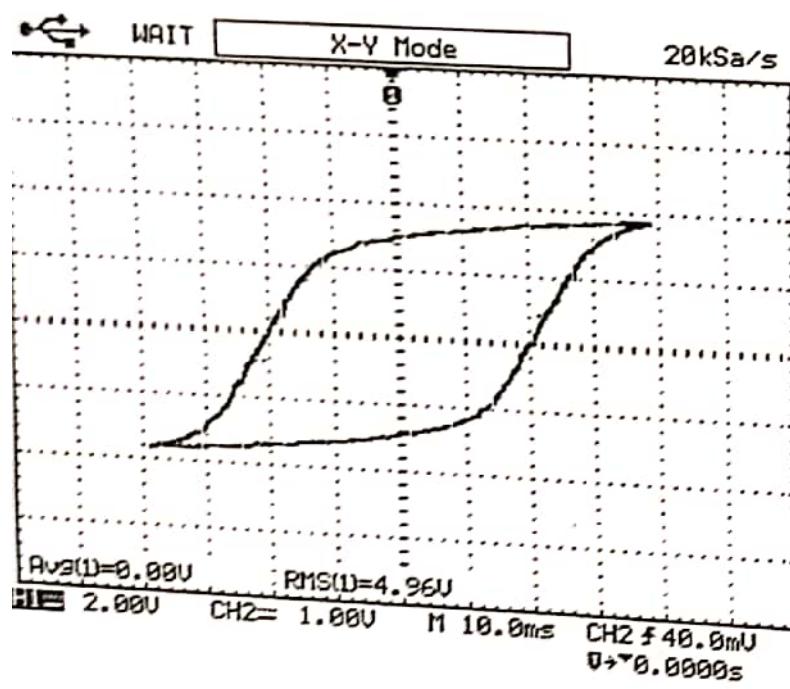

$$V = 180V$$

$$R = 36.7\Omega$$

✓

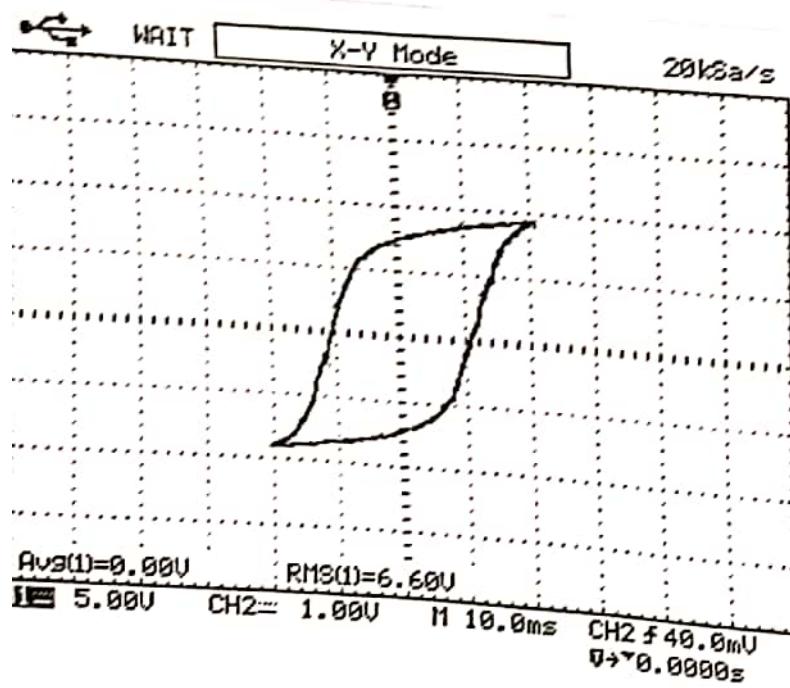

$$V = 180V$$

$$R = 49.2\Omega$$

✓

EXPERIMENT 10: SINGLE PHASE TRANSFORMER OC AND SC TEST

OBJECTIVE: To determine parameters and losses by conducting open circuit and short circuit tests on a single phase transformer.

EQUIPMENT:

- 1 Rheostat
- 2 Voltmeter (0-250V)
- 3 Ammeter (for O.C. test - 1A, for S. C. test, 0-5A)
- 4 One multi range wattmeter (0-150W)
- 5 Multimeter

OPEN CIRCUIT TEST:

PROCEDURE:

1. Make the connections as shown in the figure.
2. The secondary of transformer under test is kept open and full voltage is applied to the primary. Low current range ammeter and high voltage voltmeter are used.
3. Read the no load current, power and applied voltage.
4. Take the readings by varying the applied voltage.
5. Plot the Open Circuit Characteristic (OCC).

SHORT CIRCUIT TEST:

1. Now use the high current rating of ammeter and low voltage rating of voltmeter.
2. Short the secondary and apply the reduced voltage to the primary so that the full load current passes through the windings.

Teacher's Signature _____


3. Take the readings of voltage, current and power.
4. Take readings at 50% and 25% of rated current.
5. Plot Short Circuit Characteristic (SCC).

CALCULATIONS:

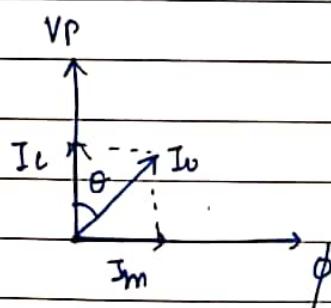(a) (i) Open circuit:-

$$P = VI \cos \theta \Rightarrow \cos \theta = \frac{P}{VI} = \frac{\text{Wattmeter reading}}{V_p \cdot I_p} = \frac{14.25 \times 2}{230 \times 0.24} = 0.516$$

$$R_c = \frac{V^2}{P} = \frac{(230)^2}{14.25 \times 2} = 18.5614 \Omega$$



$$\begin{aligned} I_m &= I_o \sin \theta \\ &= 0.24 \sin(\cos^{-1}(0.516)) \\ &= 0.205 \text{ A} \end{aligned}$$

$$X_m = \frac{V_p}{I_m} = 1121.95 \text{ j. } \Omega$$

$$X_{eff} = \sqrt{Z_{sc}^2 - R_{sc}^2} = 2.13 \Omega$$

$$(ii) R_{eff} = 2.77 \Omega$$

$$Z_{sc} = 3.45 \Omega$$

$$X_{eff} = 2.05 \Omega$$

$$(iii) R_{eff} = 2.91 \Omega$$

$$Z_{sc} = 3.5 \Omega$$

$$X_{eff} = 1.94 \Omega$$

In open circuit, $R_c \text{ avg} = 1846.82 \Omega$

$$X_m \text{ avg} = 1201.22 j \Omega$$

In short circuit, $R_{eff} \text{ (avg)} = 2.73 \Omega$

$$X_{eff} \text{ (avg)} = 2.04 j \Omega$$

RESULT: $R_c \text{ (avg)} = 1846.82 \Omega$ and $X_m \text{ avg} = 1201.22 j \Omega$ are determined by open circuit test and $R_{eff} \text{ (avg)} = 2.73 \Omega$ and $X_{eff} \text{ (avg)} = 2.04 j \Omega$ are determined by short circuit test

DISCUSSION:

Certain approximations were made while performing the tests.

1. O.C. Test: $R_s \ll R_c$, thus $I_{oc} = I_o$ (neglecting the voltage drop across series impedance)

2. S.C. Test: $I_o \ll I_{sc}$ (2-5% of I_{sc})

Thus, shunt branch parameters got neglected.

I_{sc} is rated current (4.35 A) for below.

Precautions and Sources of error:

1. Taking wattmeter reading was difficult in short circuit test due to small value.
2. Make sure that the connections were not loose.
3. Do not exceed the rated current value in S.C. test.

CONCLUSION:

Thus, circuit parameters were obtained for a single phase transformer using D.C and C.C. Test.